
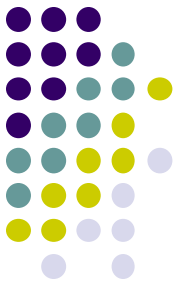


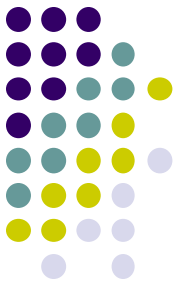Analog to Digital Converter (A/D) Digital to Analog converter (D/A)



Dr Manoj Kumar


*Department of Physics
Harishchandra P. G. College, Varanasi*




Analog signals

- Analog output is typical of most transducers and sensors.
- Need to convert these analog signals into a digital representation so the microcontroller can use it.
- Some characteristics of analog signals.
- Analog output is typical of most transducers and sensors.
- Need to convert these analog signals into a digital representation so the microcontroller can use it.

Analog signals

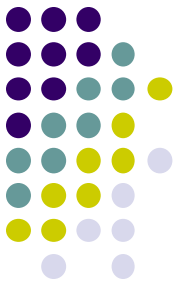

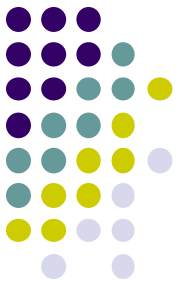
- Analog output is typical of most transducers and sensors.
- Need to convert these analog signals into a digital representation so the microcontroller can use it.
- Some characteristics of analog signals. Maximum and minimum voltages




Analog signals

- Analog output is typical of most transducers and sensors.
- Need to convert these analog signals into a digital representation so the microcontroller can use it.
- Some characteristics of analog signals.
 - Maximum and minimum voltages
 - Precise continuous signals
 - Rate of voltage change
 - Frequency if not a steady state signal

Analog-to-Digital Converters

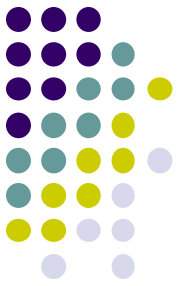

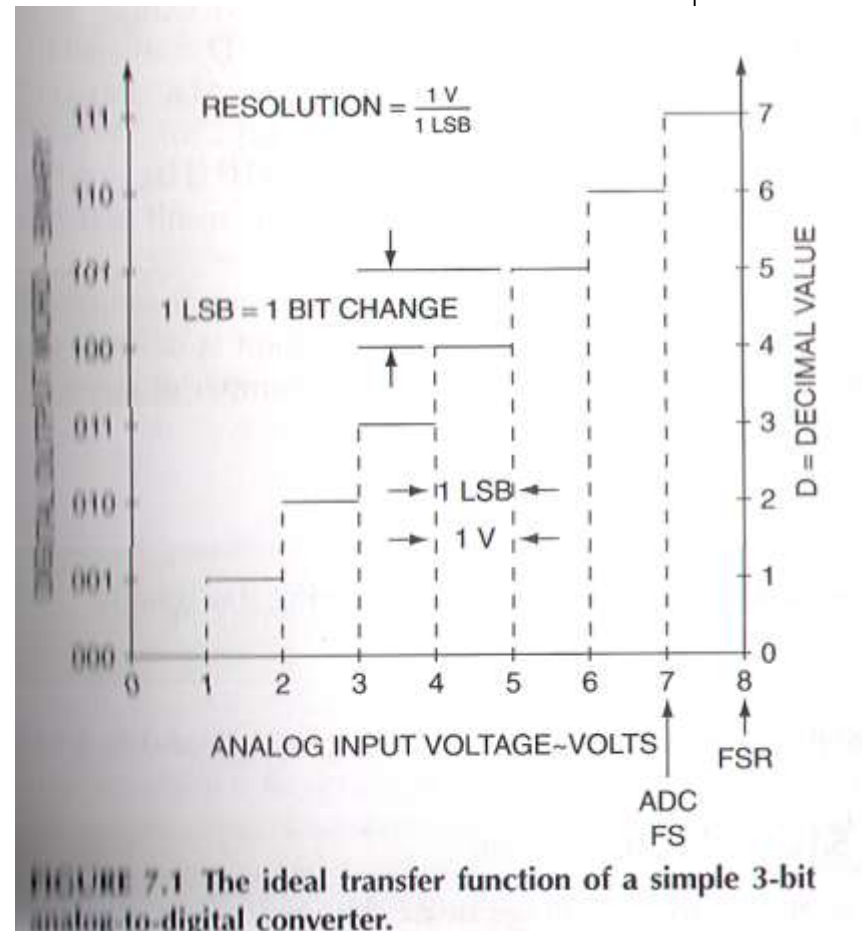- The ideal transfer function of a 3-bit ADC
- Full-scale (input voltage) range (FSR)
- Analog signal is continuous
- Digital – finite and discrete
 - In general n-bit converter
 - Total of 2^n output codes




What is a D/A ?





- A digital to analog converter (D/A) converts a digital signal to an analog voltage or current output.

100101...

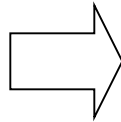

DAC

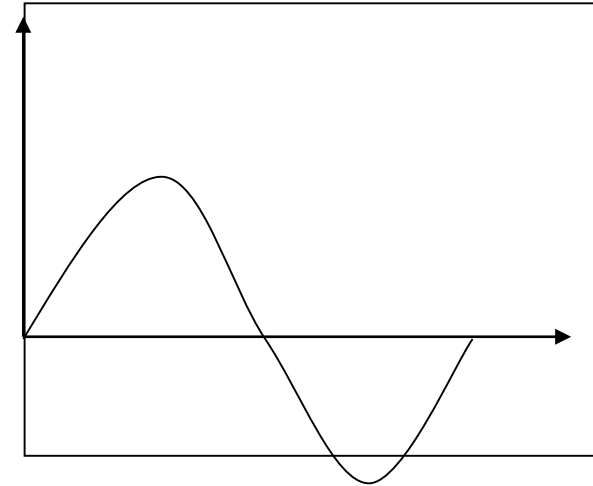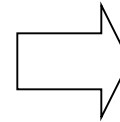

Types of D/A



- Many types of D/A available.
- Usually switches, resistors, and op-amps used to implement conversion
- Two Types:
 - Binary Weighted Resistor
 - R-2R Ladder

Binary Weighted Resistor

- Utilizes a summing op-amp circuit
- Weighted resistors are used to distinguish each bit from the most significant to the least significant
- Transistors are used to switch between V_{ref} and ground (bit high or low)



Binary Weighted Resistor


- Assume Ideal Op-amp
- No current into op-amp
- Virtual ground at inverting input
- $V_{out} = -IR_f$

If $R_f = R/2$

$$V_{out} = -IR_f = -\left(\frac{V_1}{2} + \frac{V_2}{4} + \frac{V_3}{8} + \dots + \frac{V_n}{2^n}\right)$$

For example, a 4-Bit converter yields
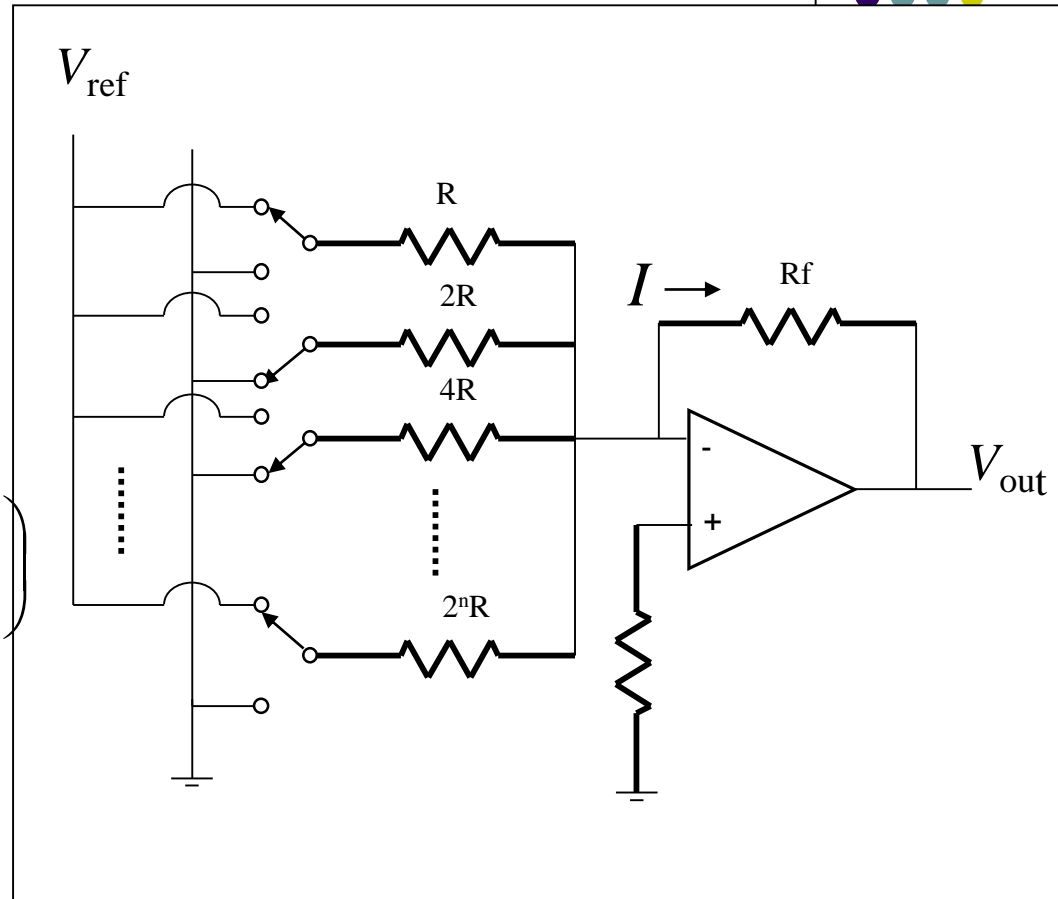
$$V_{out} = -V_{ref} \left(b_3 \frac{1}{2} + b_2 \frac{1}{4} + b_1 \frac{1}{8} + b_0 \frac{1}{16} \right)$$



Where b_3 corresponds to Bit-3, b_2 to Bit-2, etc.

Binary Weighted Resistor




Voltages V_1 through V_n are either V_{ref} if corresponding bit is high or ground if corresponding bit is low

V_1 is most significant bit

V_n is least significant bit
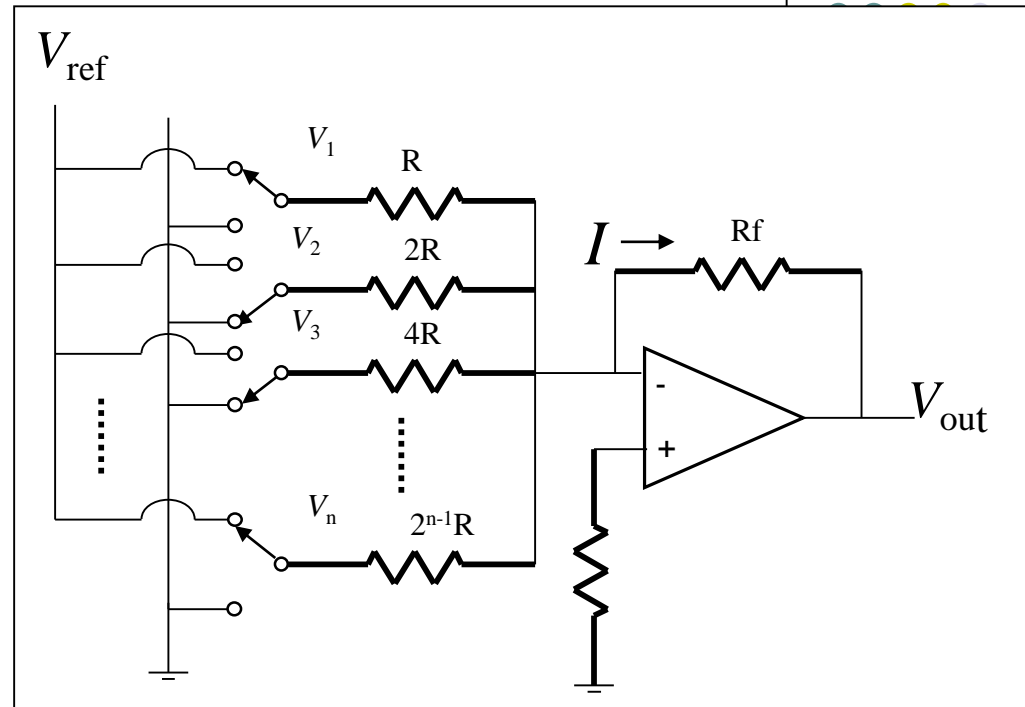
$$V_{out} = -IR_f = -R_f \left(\frac{V_1}{R} + \frac{V_2}{2R} + \frac{V_3}{4R} + \dots + \frac{V_n}{2^{n-1}R} \right)$$





- Advantages

- Simple Construction/Analysis
- Fast Conversion

- Disadvantages

- Requires large range of resistors (2000:1 for 12-bit DAC) with necessary high precision for low resistors
- Requires low switch resistances in transistors
- Can be expensive. Therefore, usually limited to 8-bit resolution.

R-2R Ladder


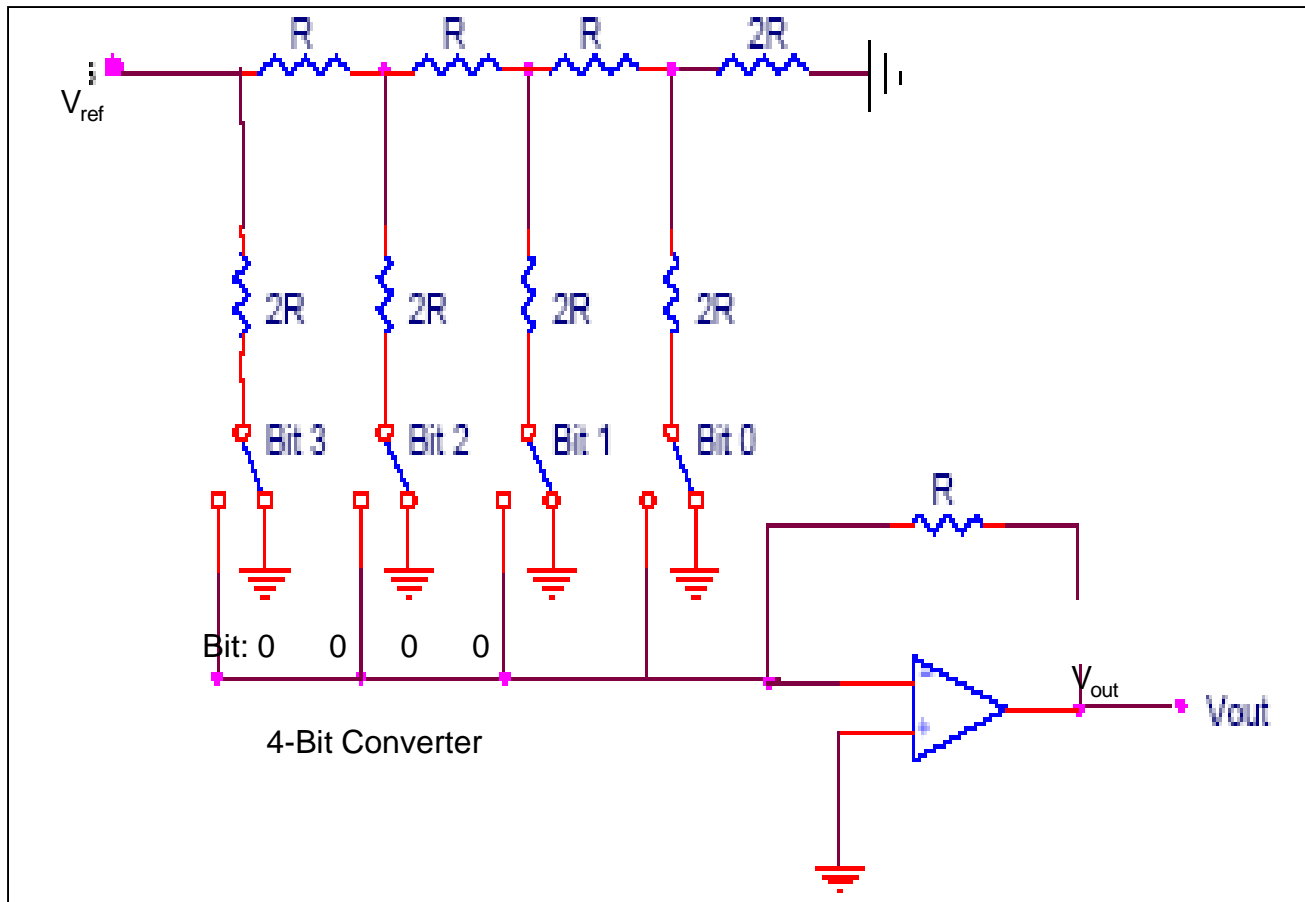
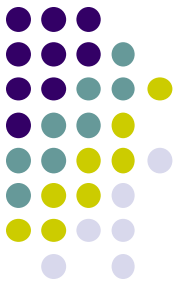


Each bit corresponds to a switch:

If the bit is high, the corresponding switch is connected to the inverting input of the op-amp.




If the bit is low, the corresponding switch is connected to ground.

R-2R Ladder

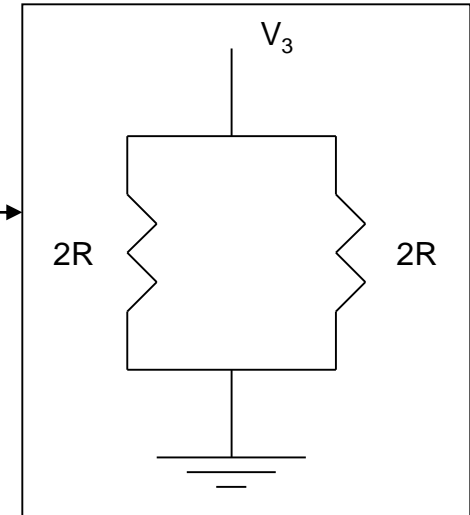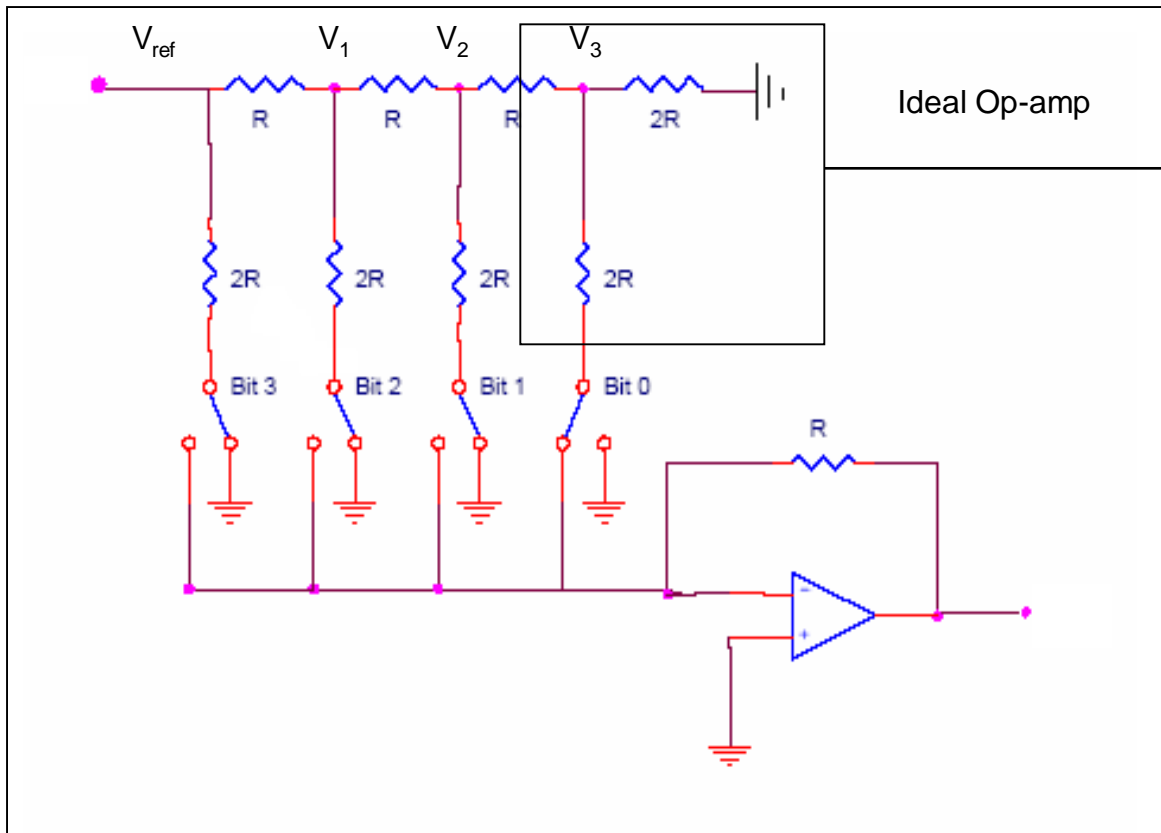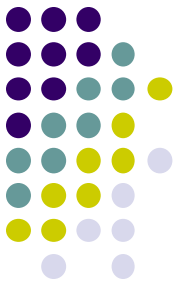

$$R_{eq} = \frac{(2R)(2R)}{(2R + 2R)} = R$$

R-2R Ladder

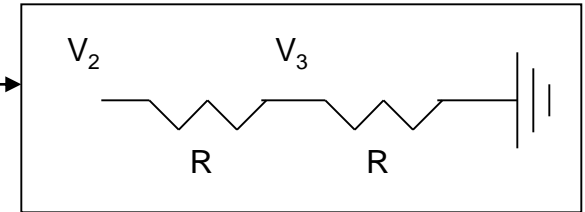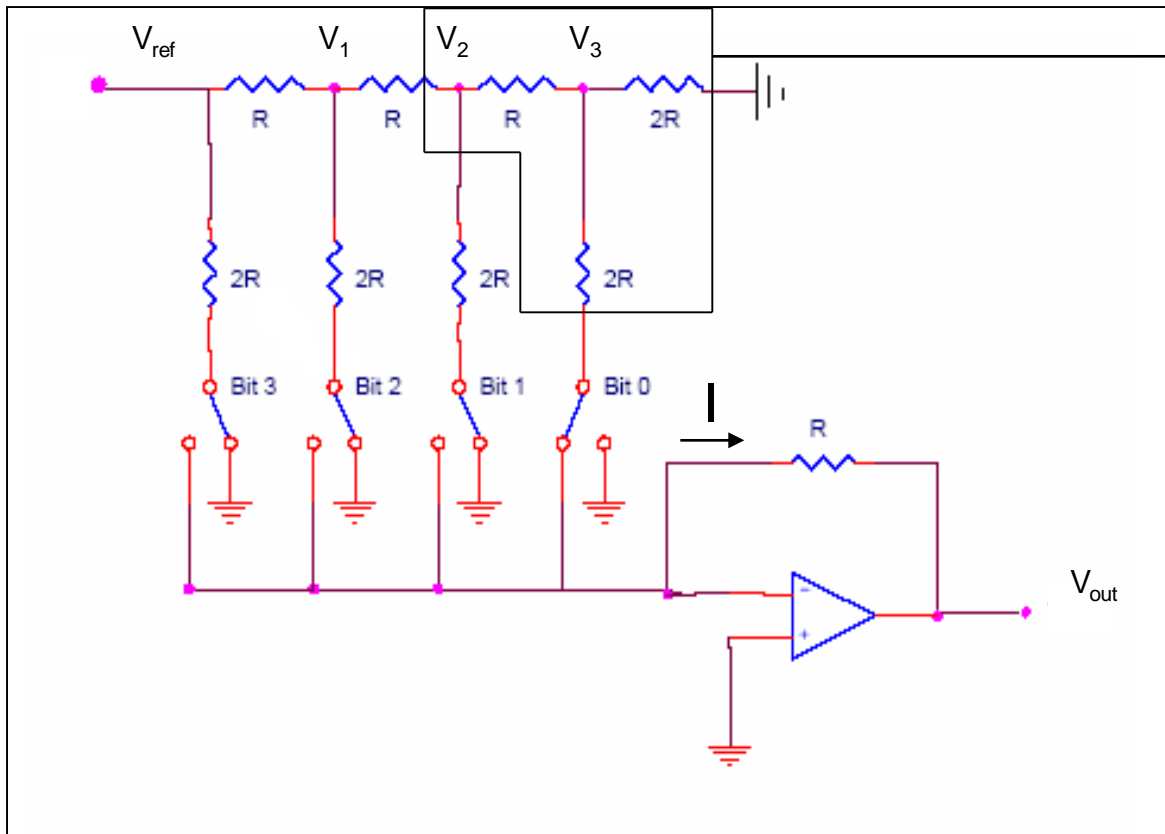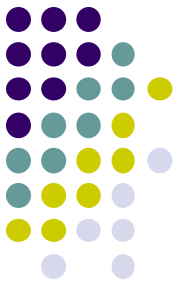

$$V_3 = \left(\frac{R}{R + R} \right) V_2 = \frac{1}{2} V_2$$


Likewise,

$$V_2 = \frac{1}{2} V_1$$

$$V_1 = \frac{1}{2} V_{\text{ref}}$$

$$V_{\text{out}} = -IR$$

R-2R Ladder

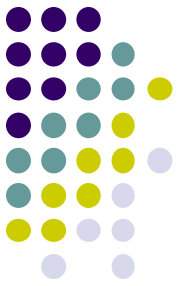

Results:


$$V_3 = \frac{1}{8} V_{\text{ref}}, V_2 = \frac{1}{4} V_{\text{ref}}, V_1 = \frac{1}{2} V_{\text{ref}}$$

$$V_{\text{out}} = -R \left(b_3 \frac{V_{\text{ref}}}{2R} + b_2 \frac{V_{\text{ref}}}{4R} + b_1 \frac{V_{\text{ref}}}{8R} + b_0 \frac{V_{\text{ref}}}{16R} \right)$$

Where b_3 corresponds to bit 3,
 b_2 to bit 2, etc.

If bit n is set, $b_n=1$

If bit n is clear, $b_n=0$

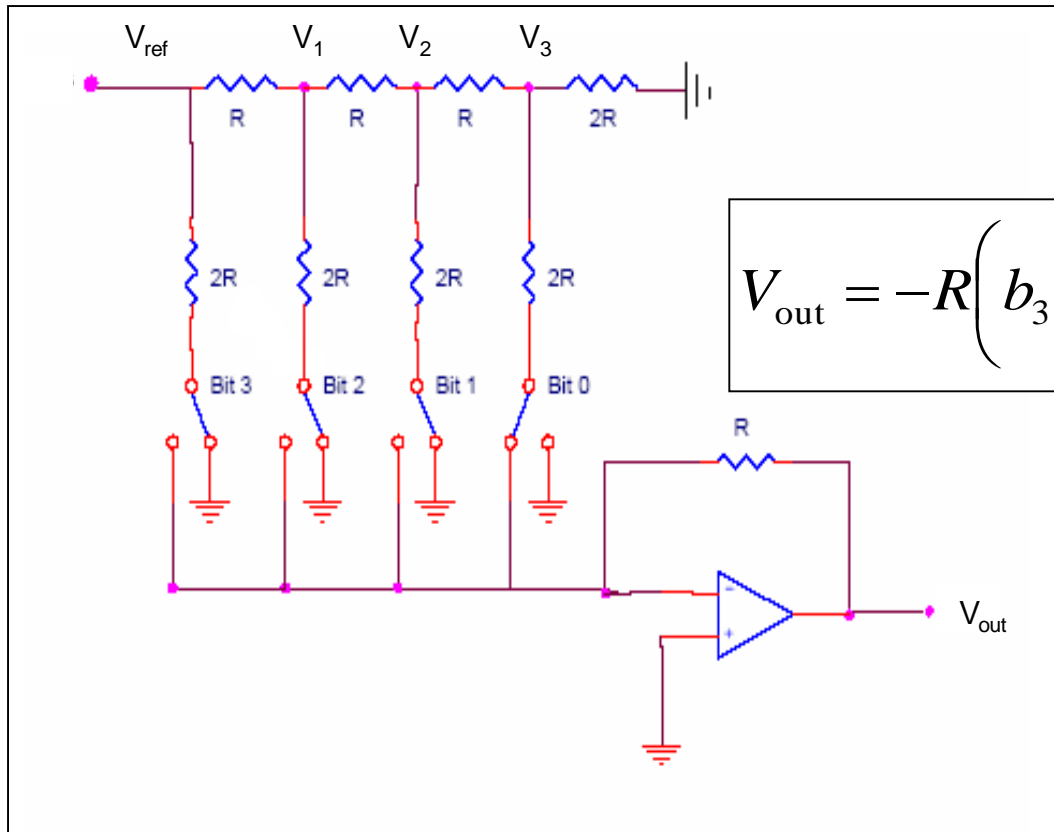

R-2R Ladder

For a 4-Bit R-2R Ladder

$$V_{\text{out}} = -V_{\text{ref}} \left(b_3 \frac{1}{2} + b_2 \frac{1}{4} + b_1 \frac{1}{8} + b_0 \frac{1}{16} \right)$$

For general n-Bit R-2R Ladder or Binary Weighted Resistor DAC

$$V_{\text{out}} = -V_{\text{ref}} \sum_{i=1}^n b_{n-i} \frac{1}{2^i}$$

- Advantages

- Only two resistor values (R and 2R)
- Does not require high precision resistors

- Disadvantage

- Lower conversion speed than binary weighted DAC